 


國立清華大學 電機工程學系  
111 學年度第二學期  
**EE-6250 超大型積體電路測試 VLSI Testing**  
**Homework #1 (佔學期總成績 10 分)**

(每人一組) Due Date : **23:59pm, March 20 (Monday), 2023**, (逾時不收)  
Submission to <https://eeclass.nthu.edu.tw/> 作業區

1. Consider the testing of a gate-level circuit as shown below. The primary input signals are  $\{x1, x2, x3\}$  and the primary output signal is  $\{z\}$ . The output signals of logic gates  $\{A, B\}$  are denoted as  $\{a, b\}$ , and the branches of primary input signal  $x2$  is called  $y1$  and  $y2$ , respectively.



- (a) (50%) Write a software program (using C, C++, or any other programming language) that can **exhaustively simulate the logic behavior of the given circuit** under each of the  $2^3 = 8$  input vectors). Note that this can be done by executing the following Boolean equations in sequence in your program:

$a = \sim(x1 \text{ or } x2);$   
 $b = \sim(x2 \text{ and } x3);$   
 $z = (a \text{ or } b);$

List the results as a truth table for output signal  $z$ . (Note this truth table contains 8 entries, one for each input combination).

- (b) (50%) Enhance your program so that it can perform **exhaustive fault simulation for bridging faults**,  $\{AND\text{-bridging between } a \text{ and } b\}$  and  $\{OR\text{-bridging between } y1 \text{ and } x3\}$ . Note that you need to report the total number of possible test patterns for each of the above two bridging faults. (Hint: perform fault injection, run exhaustive simulation on the faulty circuit, and then compare the results with those of the fault-free circuit. The fault injection can be done **manually** by changing the compiled code.)

**Note: 繳交資料:** (1) Combine your answers to the above questions (a)-(b) into a single PDF file. (2) Append to the above combined file your source code of your C or C++ program. (3) Attach a cover page with your 系所, 中英文姓名, 學號等資訊 before submitting your all-in-one file to our **【清華大學-數位學習平台】** (<https://eeclass.nthu.edu.tw/>).